




Hector Latorre, ABB FACTS, 2016-11-24

TCSC Introduction and its capability on SSR Mitigation

500 kV TCSC




TCSC Single Line Diagram

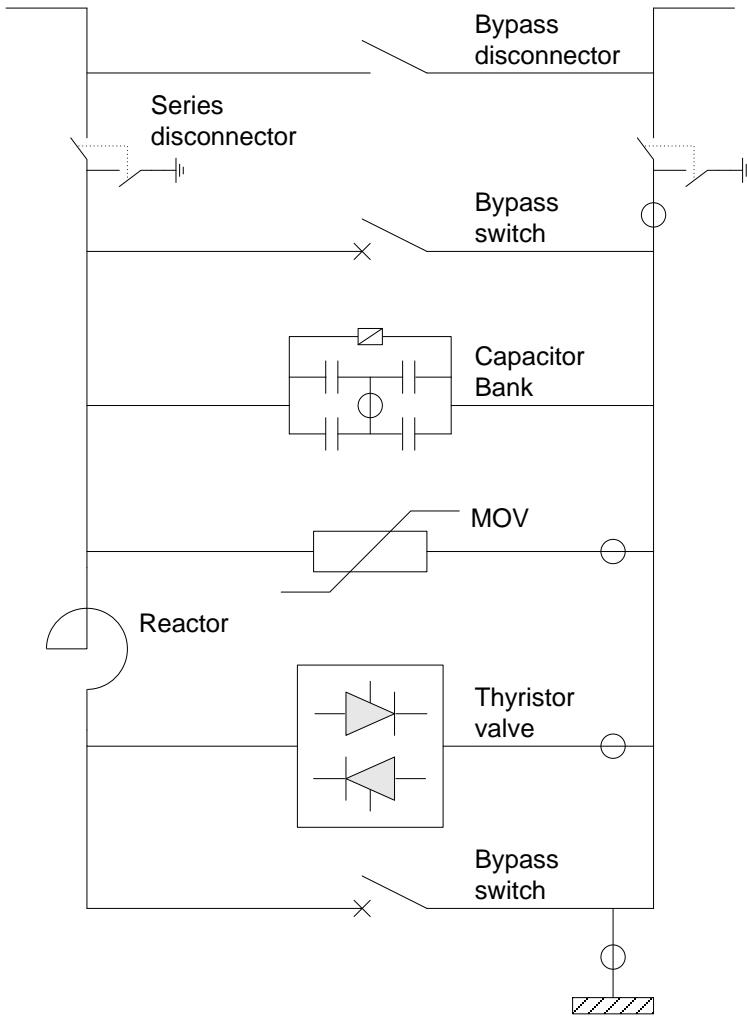

TCSC

Operational objectives

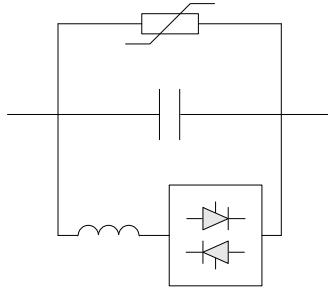- Thyristor Controlled Series Compensations (TCSC)



- Subsynchronous resonance (SSR) mitigation,
- Power oscillation damping,
- Transient stability
- Current (power flow) control,
- Voltage control (reactance control),
- Phase balancing control

TCSC

Main components

- **Capacitor bank:**
compensation degree given by the customer
- **MOV:**
study performed as a FSC
- **Reactor:**
determined by the factor λ


$$\lambda = \frac{\omega_0}{\omega_N} \quad \lambda = \sqrt{\frac{X_C}{X_L}}$$

- λ can be between 2 and 4. Typical values: 2.5 and 3.5
- **Thyristor valves:**
Number of thyristors is mainly a function of the capacitor voltage at triggering instant and protective level

TCSC

Steady state operation



- Currents in TCSC circuit

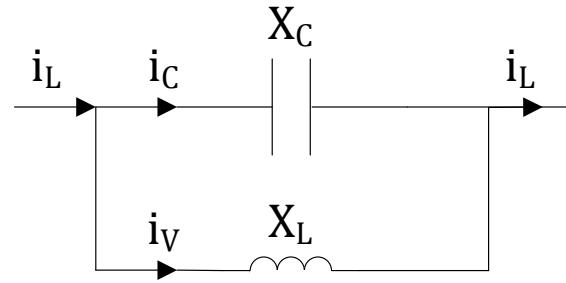



$$i_V = i_L \frac{-jX_C}{j(X_L - X_C)}$$

$$i_C = i_L \frac{-jX_L}{j(X_L - X_C)}$$

TCSC Operation Blocked mode

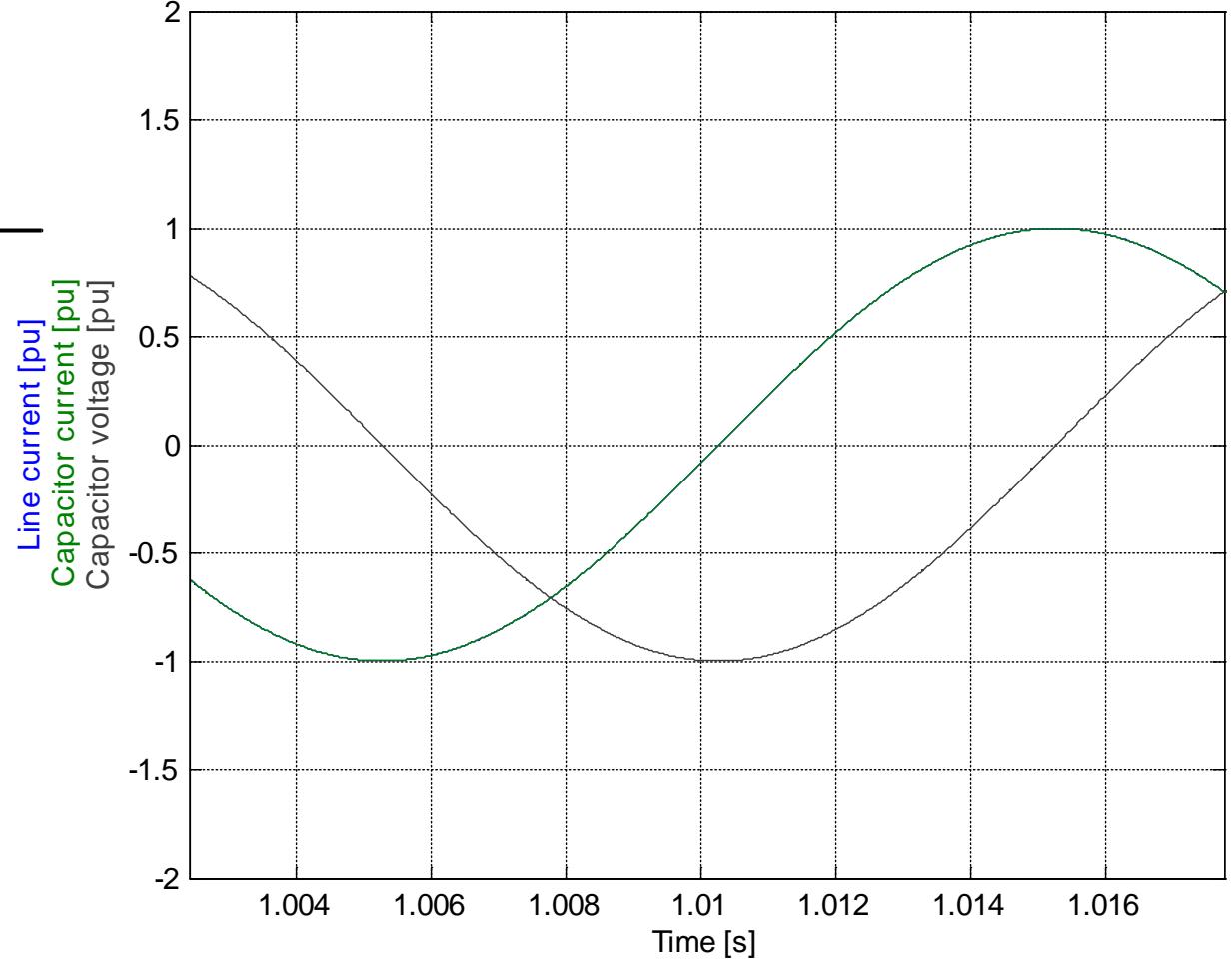
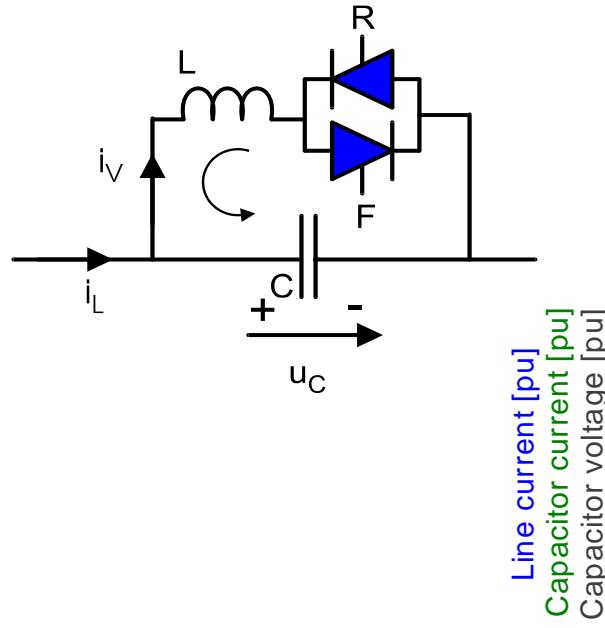


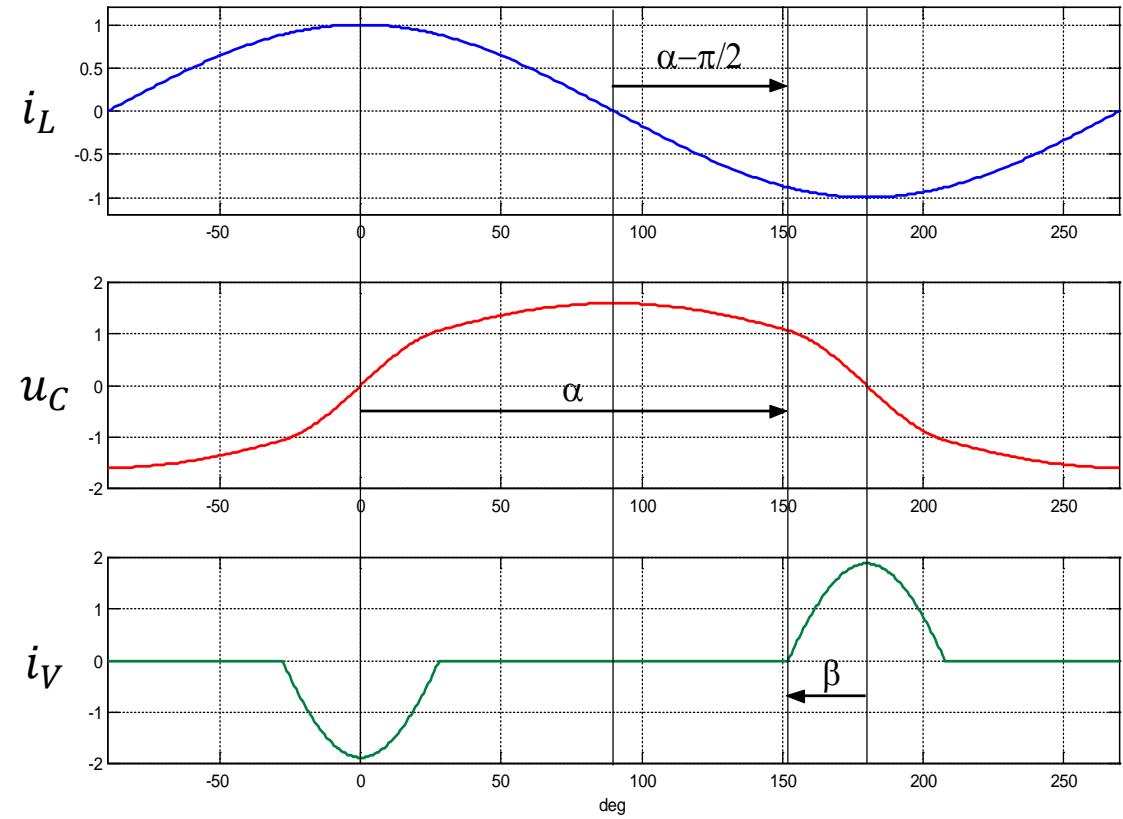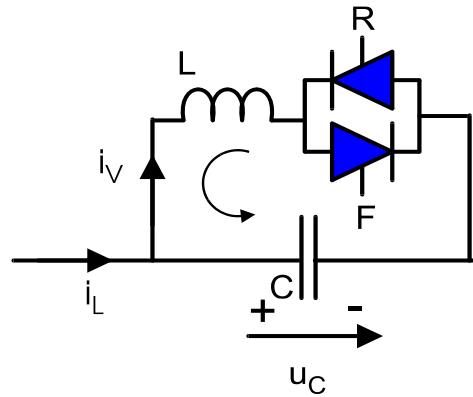TCSC Operation Capacitive (boost or Vernier) mode



TCSC Operation


Capacitive (boost or Vernier) mode

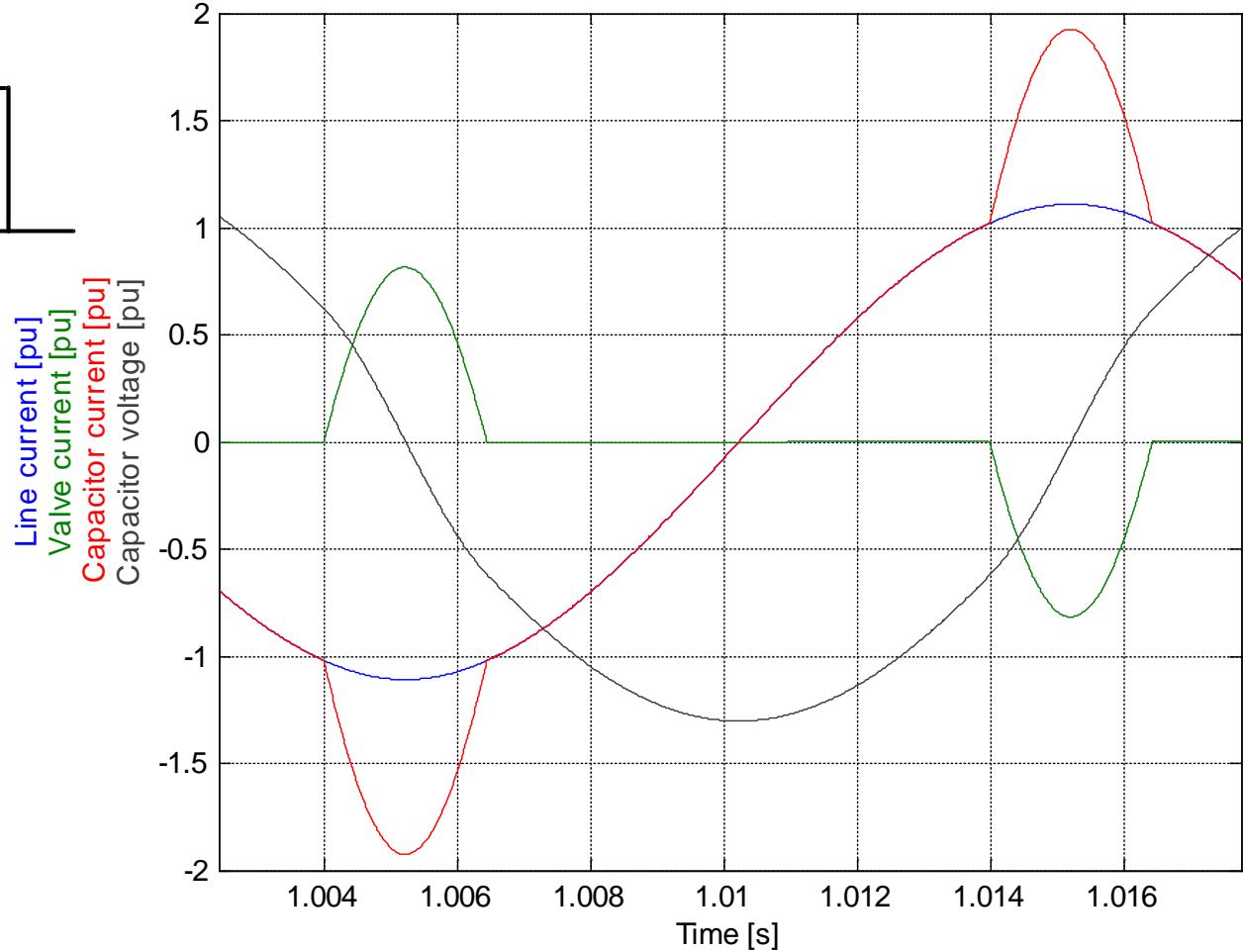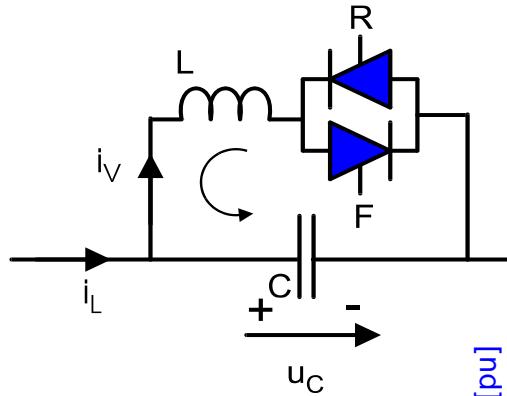


Boost factor:

$$k_B = \frac{\hat{M}_{app}}{\hat{X}_{app}}$$


Operation in CAP mode

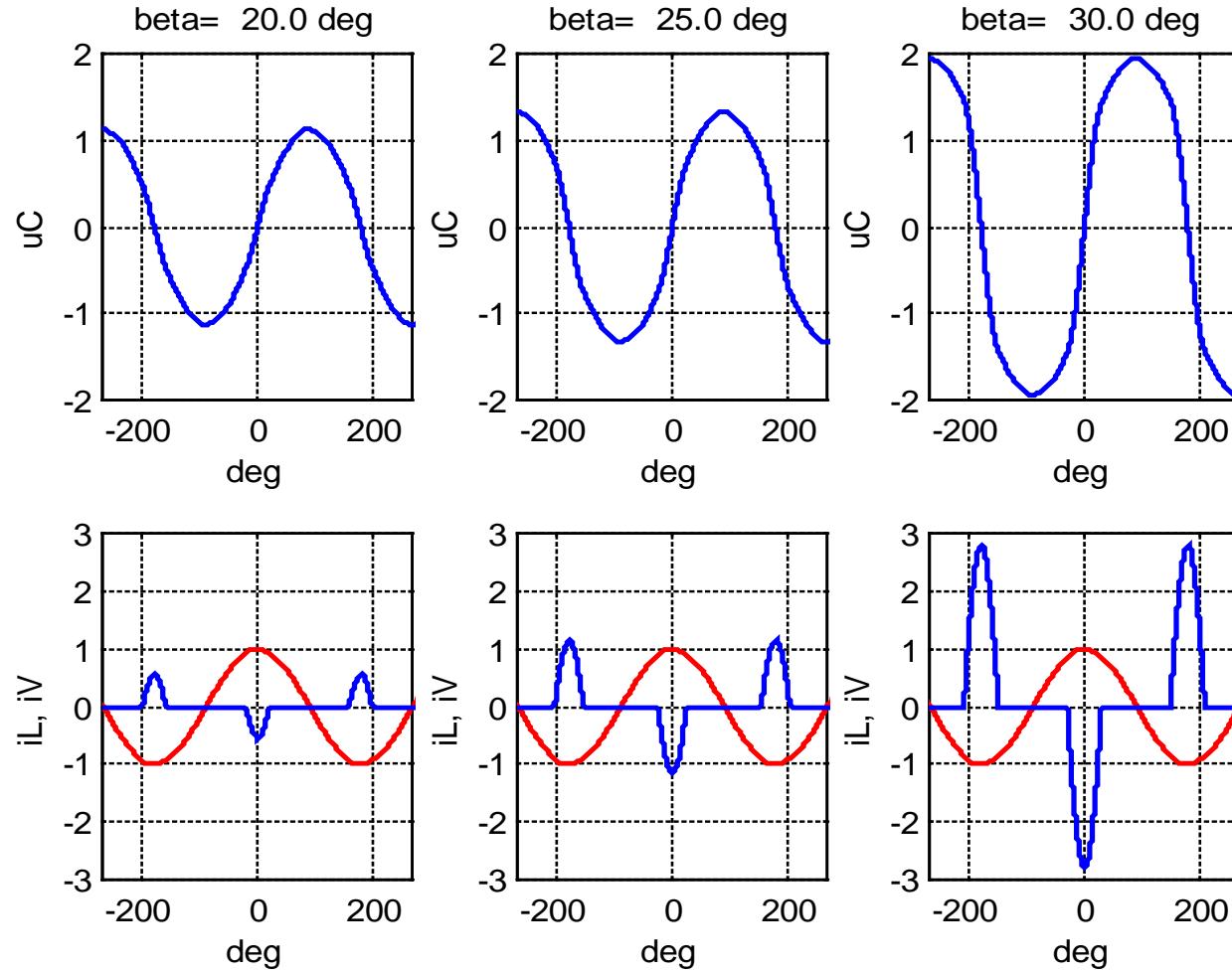

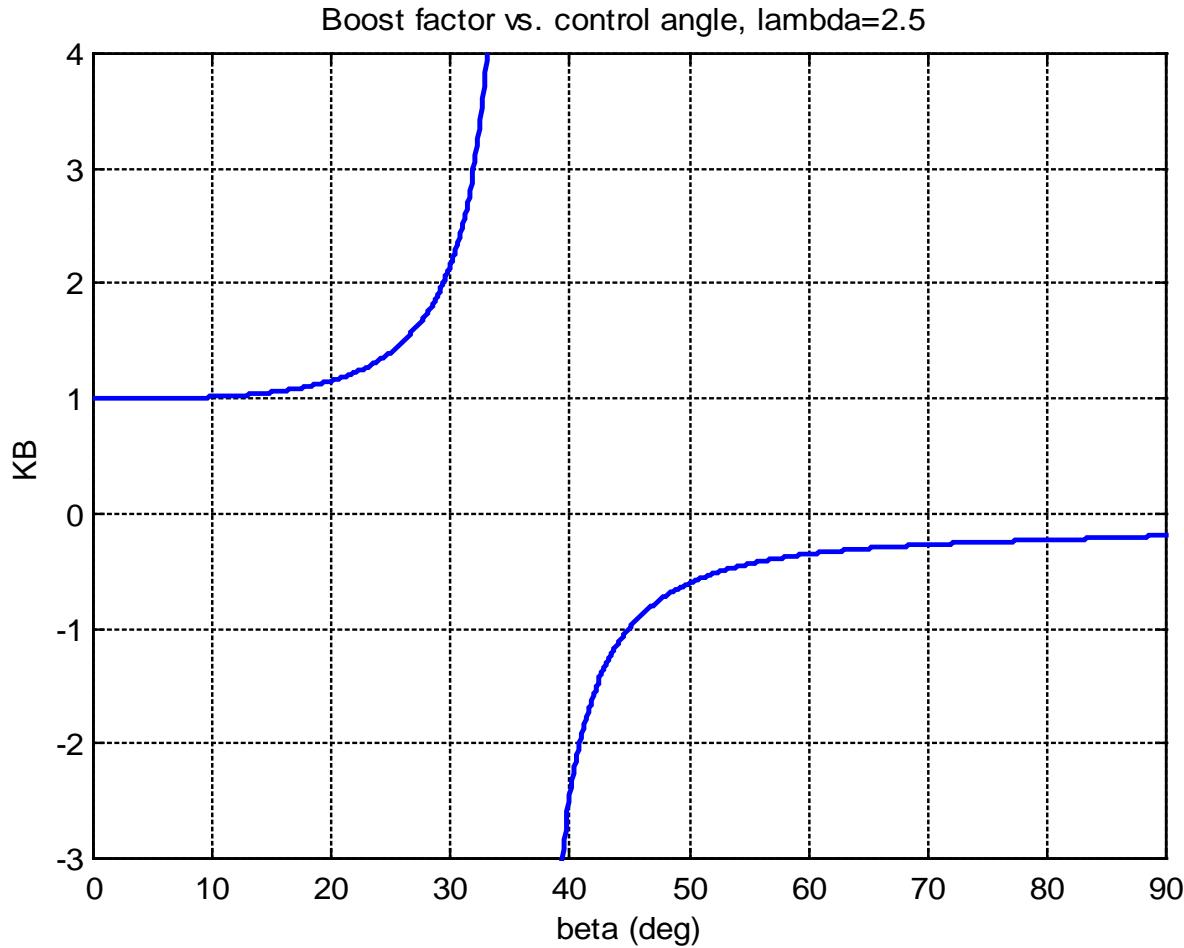
Steady state relation between firing angle and kB





Typical operating range for POD

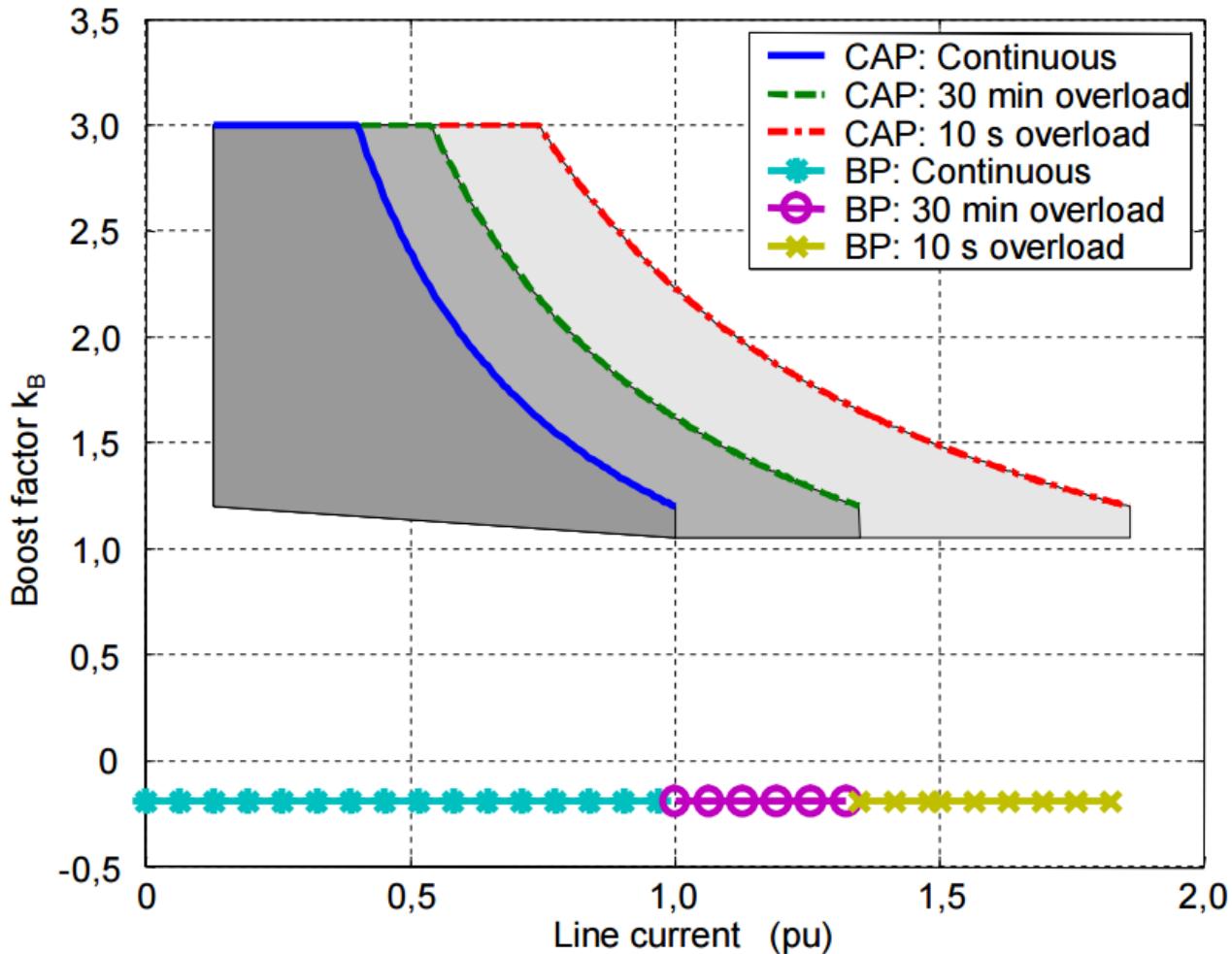


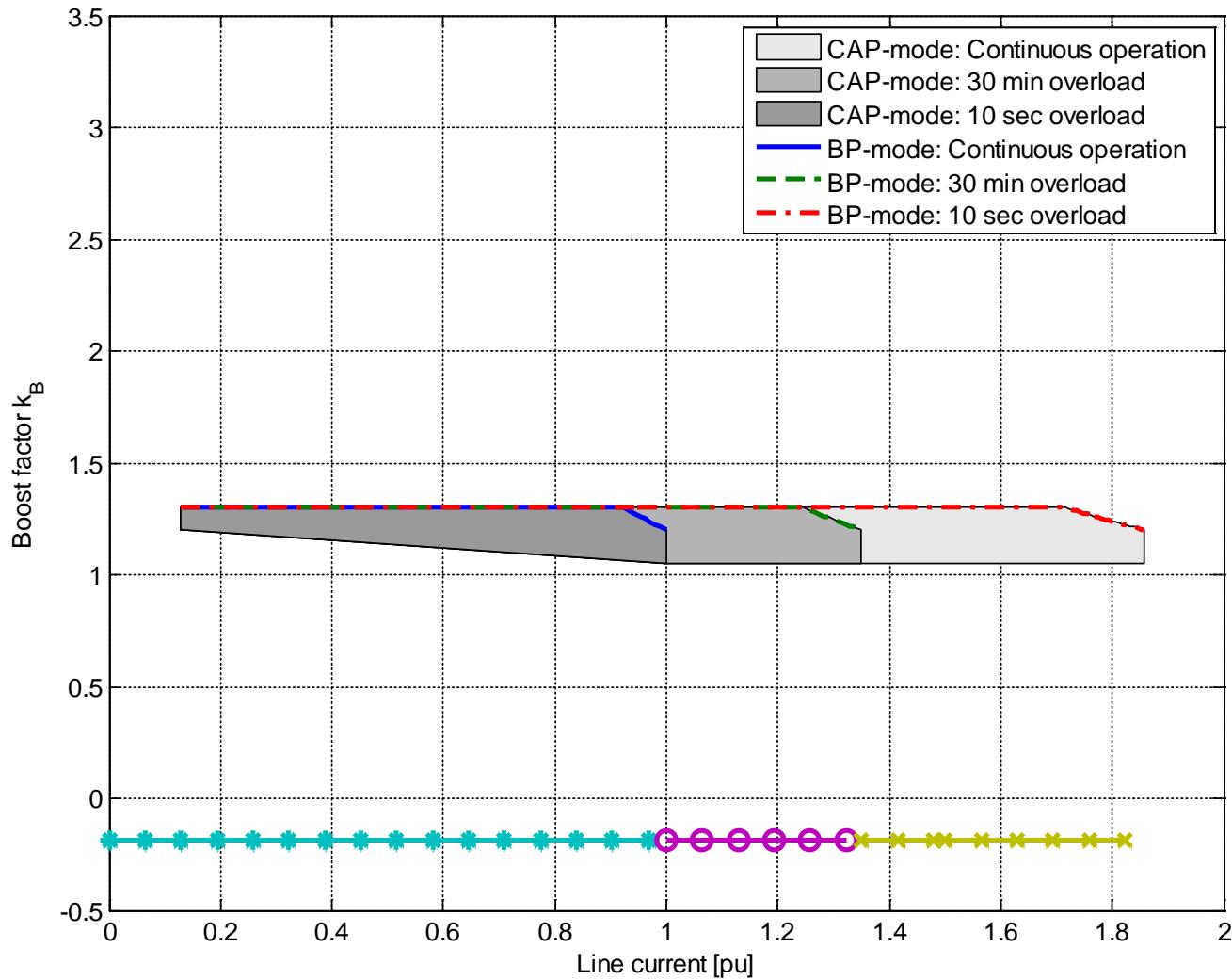
Typical operating range for SSR mitigation



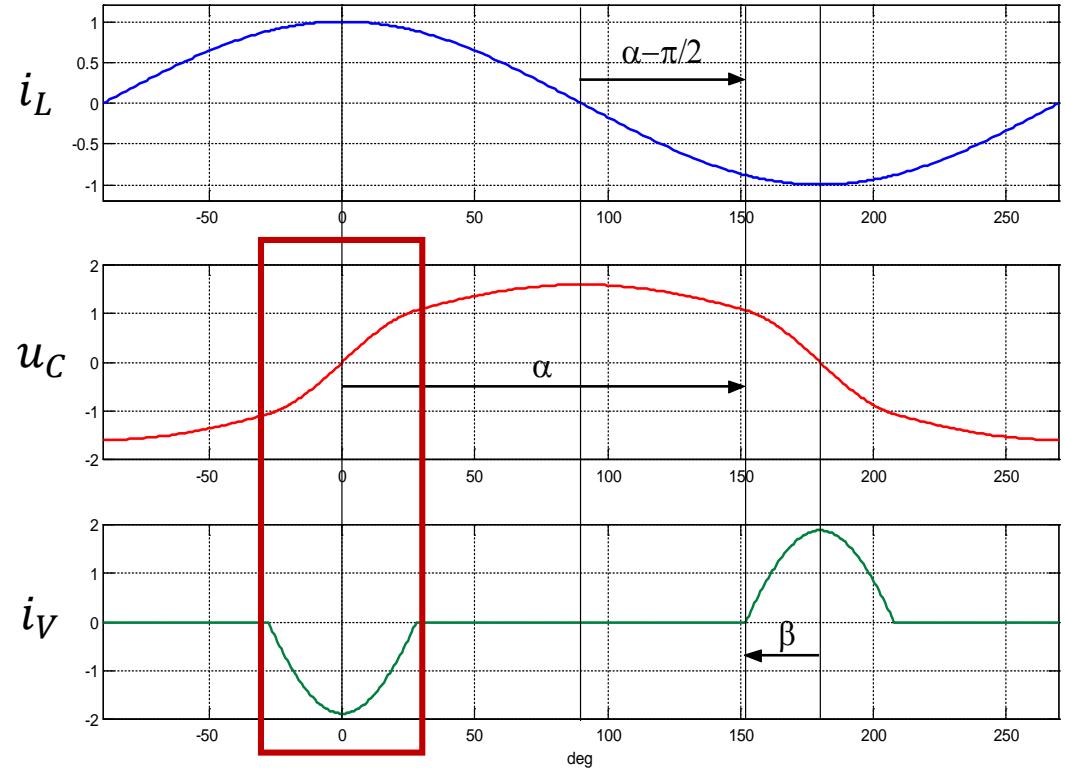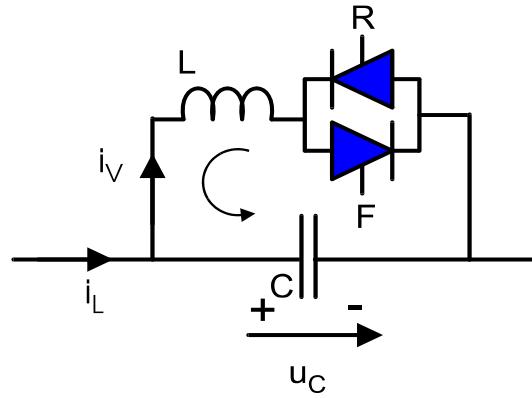
TCSC Control Synchronous Voltage Reversal



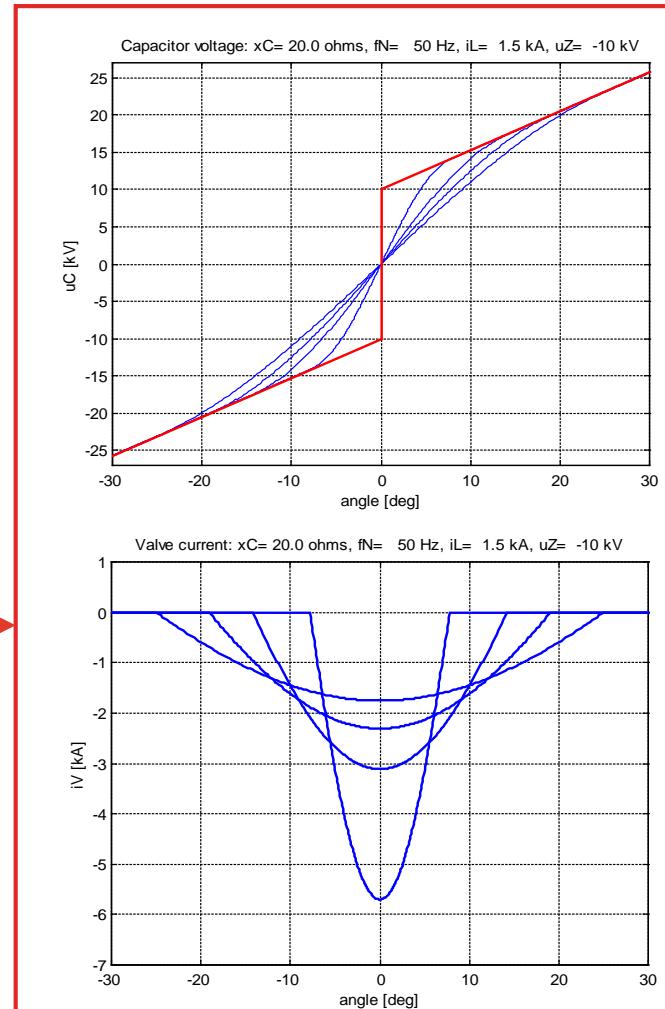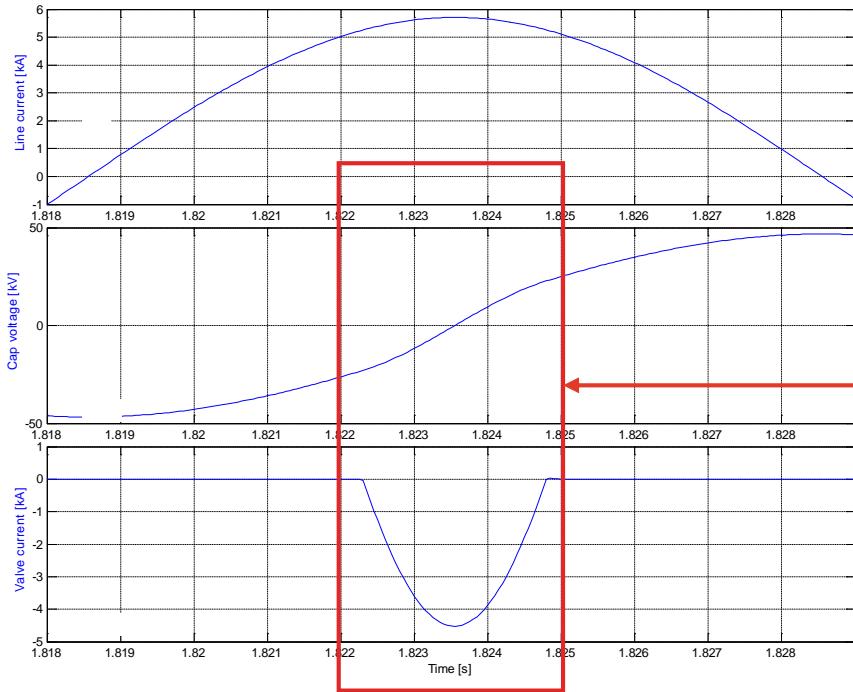
Synchronous Voltage Reversal Thyristor action



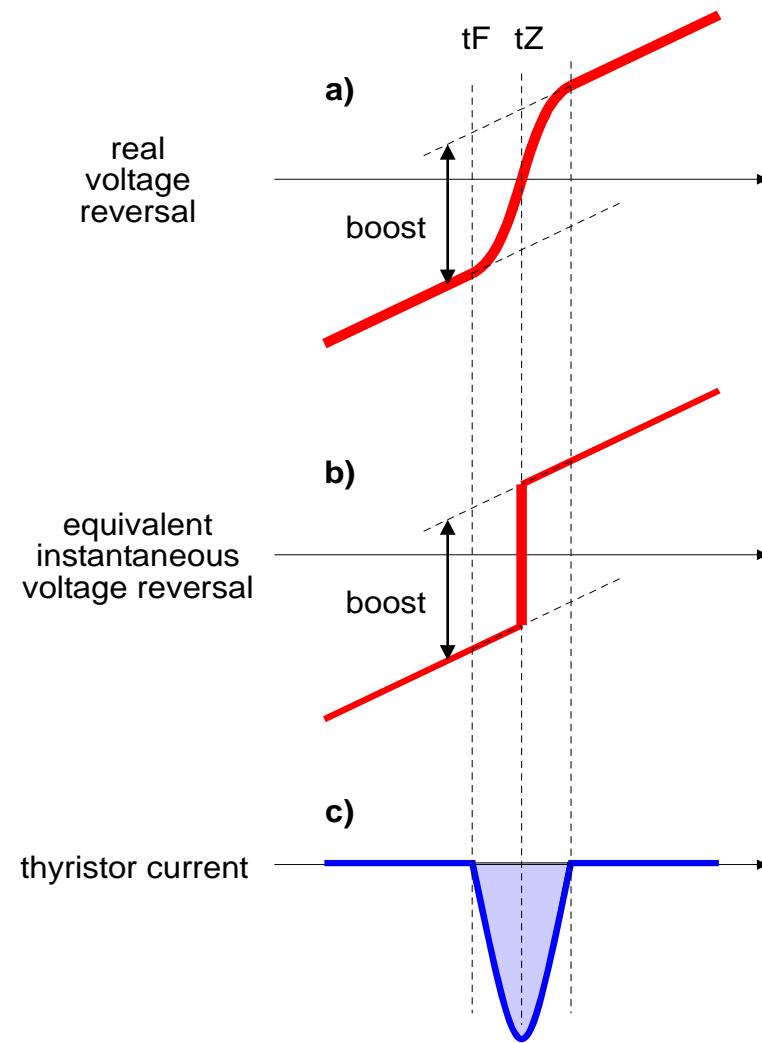
Equivalent instantaneous voltage reversal




Idealized steady-state voltage

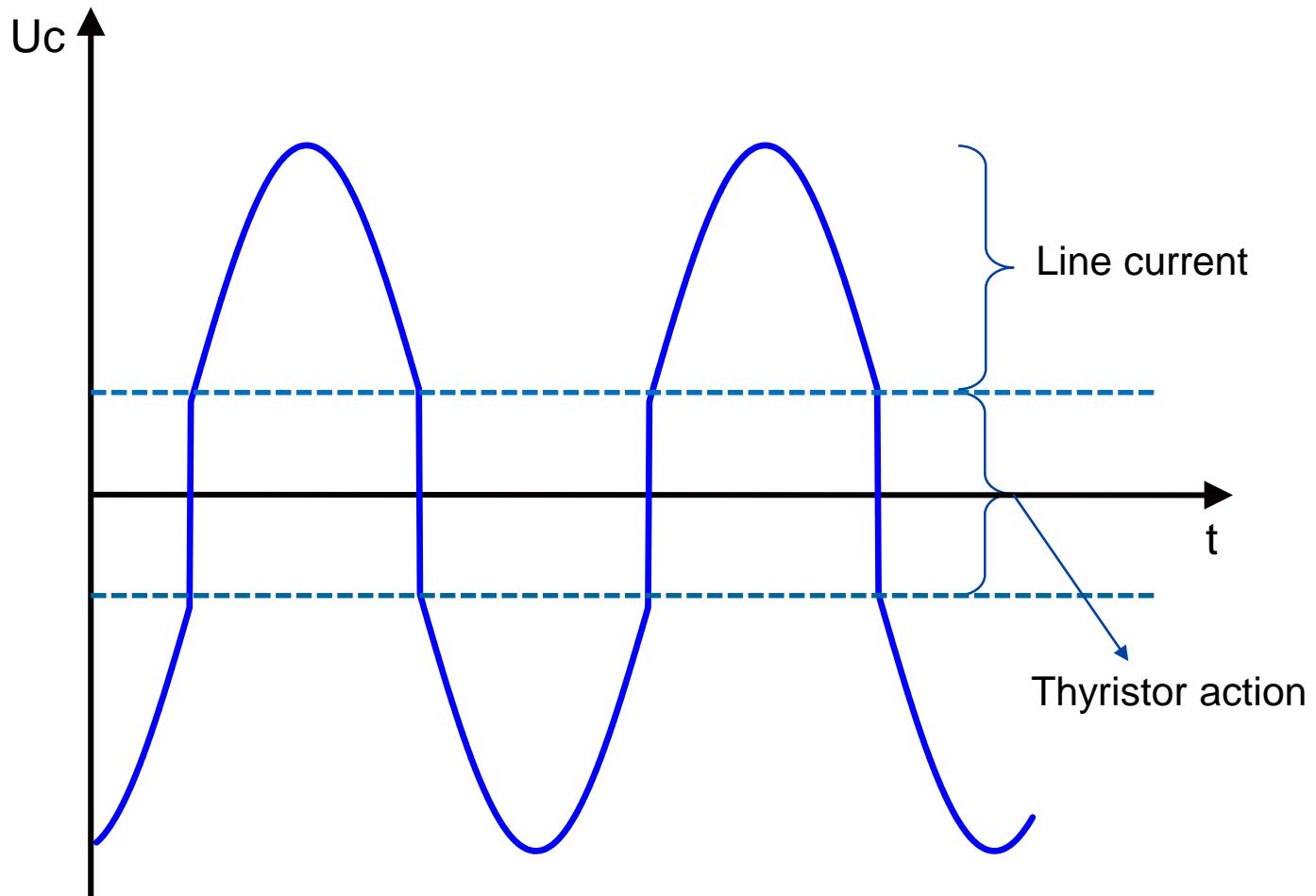

Boost control

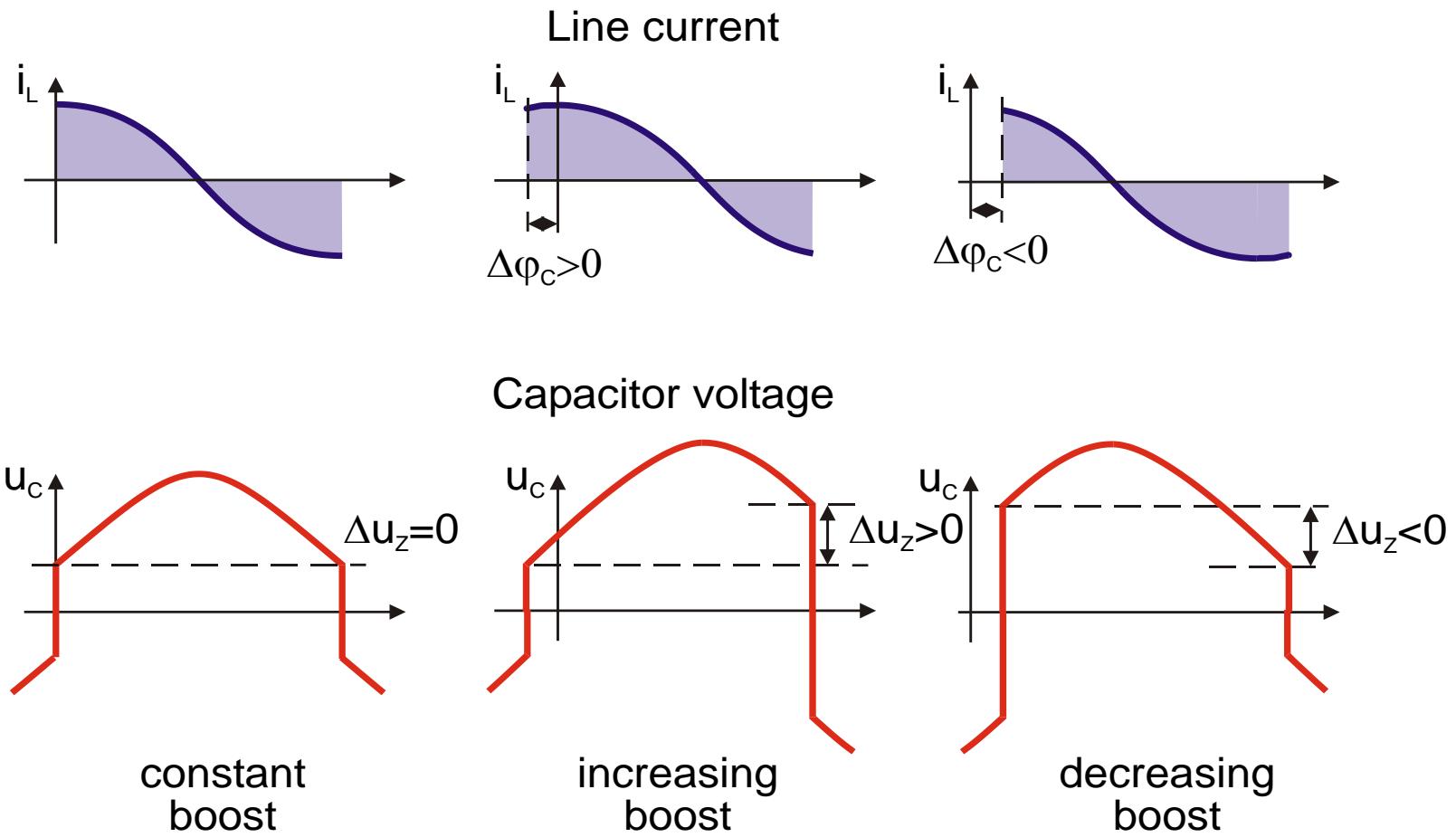


Outline TCSC control

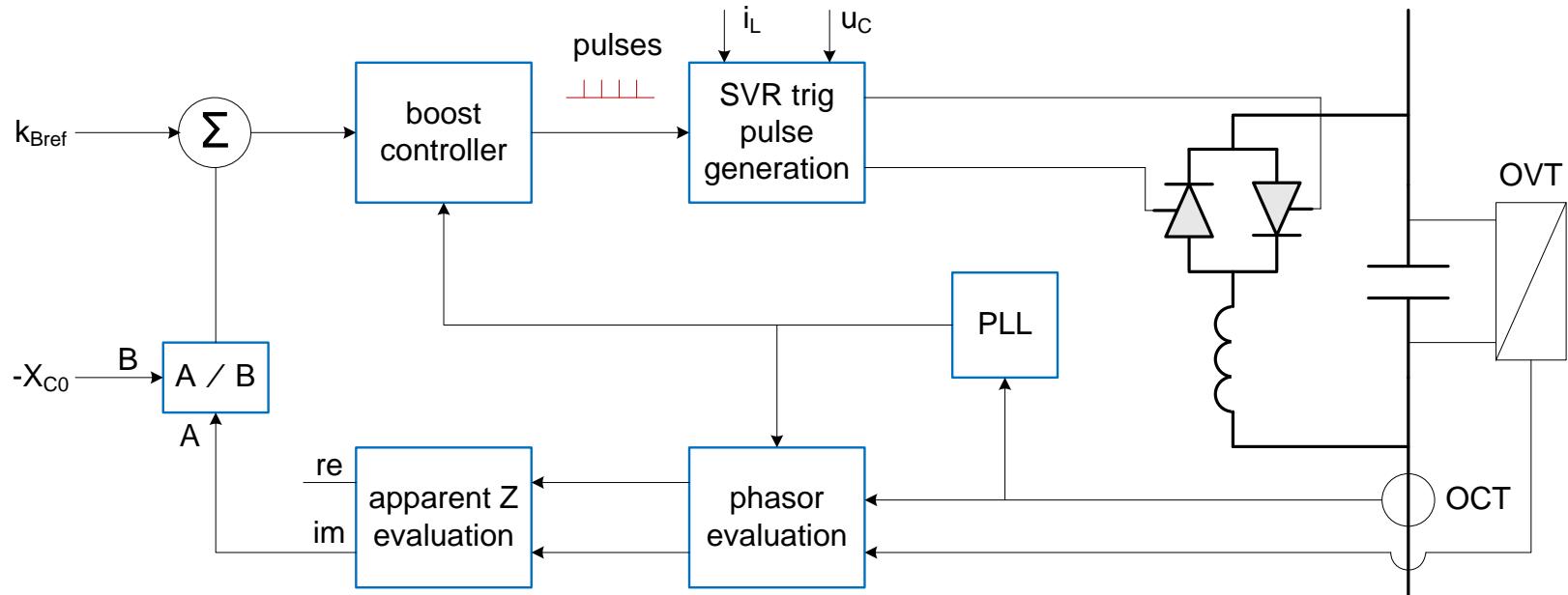

OCT: Optical Current Transducer

OVT: Optical Voltage Transducer


Apparent impedance

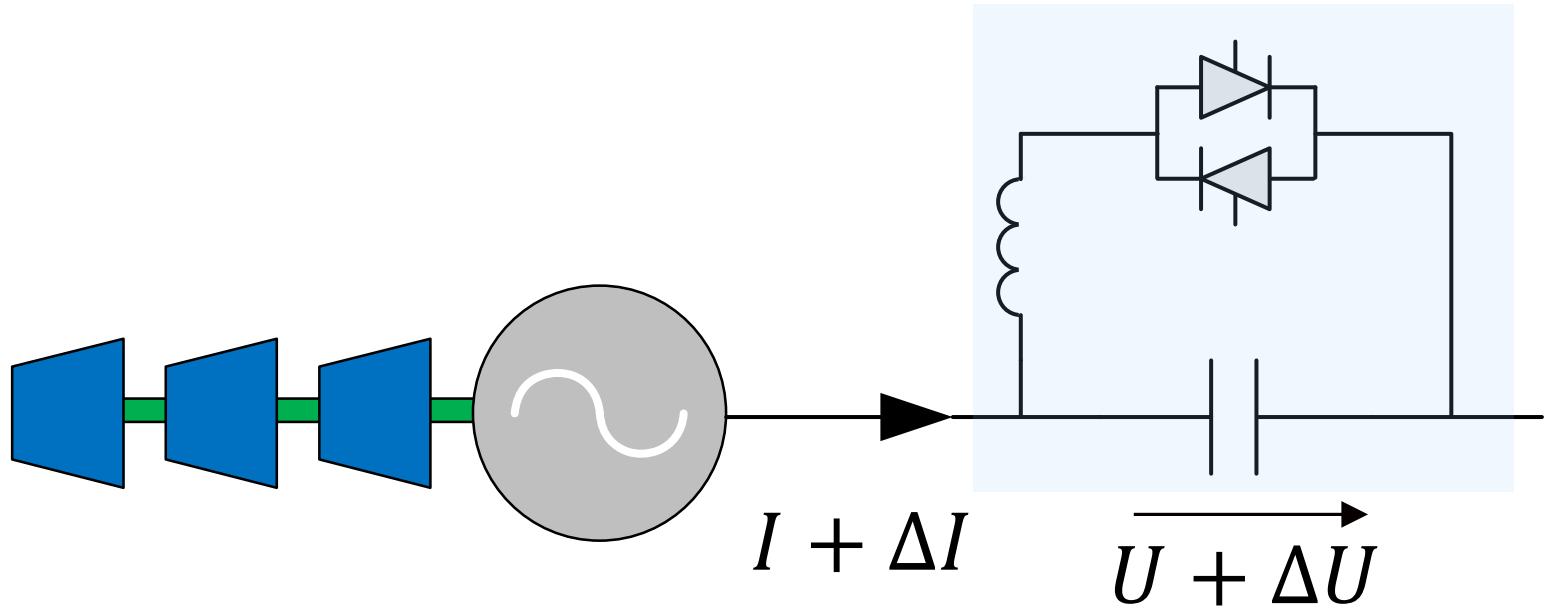

$$Z_{app} = \frac{\Delta U}{\Delta I}$$


Apparent impedance for FSC and TCSC

fixed series capacitor

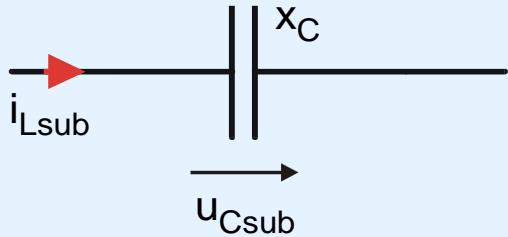


$$z_{app} = \frac{u_{Csub}}{i_{Lsub}} = -j \frac{f_N}{f_{sub}} x_C$$

TCSC

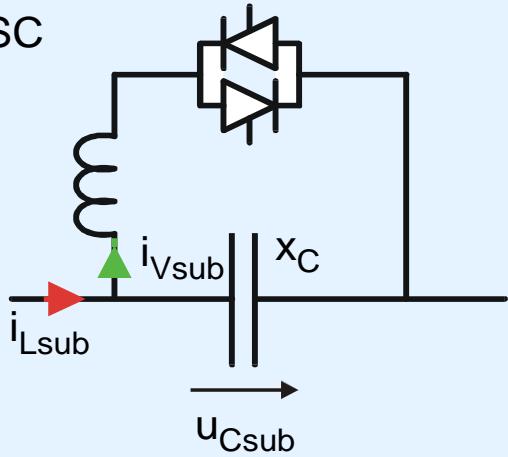


$$z_{app} = \frac{u_{Csub}}{i_{Lsub}} = -j \frac{f_N}{f_{sub}} \frac{i_{Lsub} - i_{Vsub}}{i_{Lsub}} x_C = ?$$


10 Hz current in a fixed SC

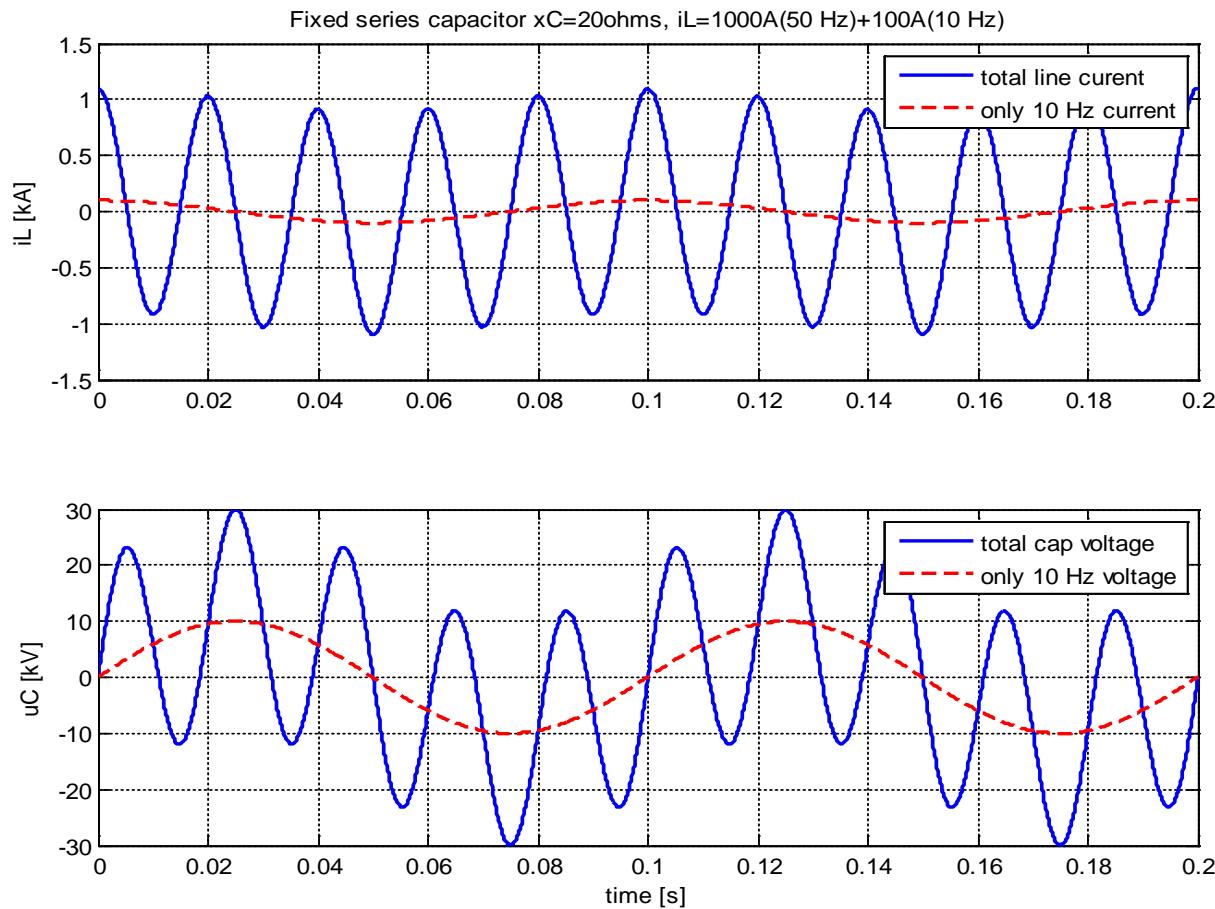


DC injection

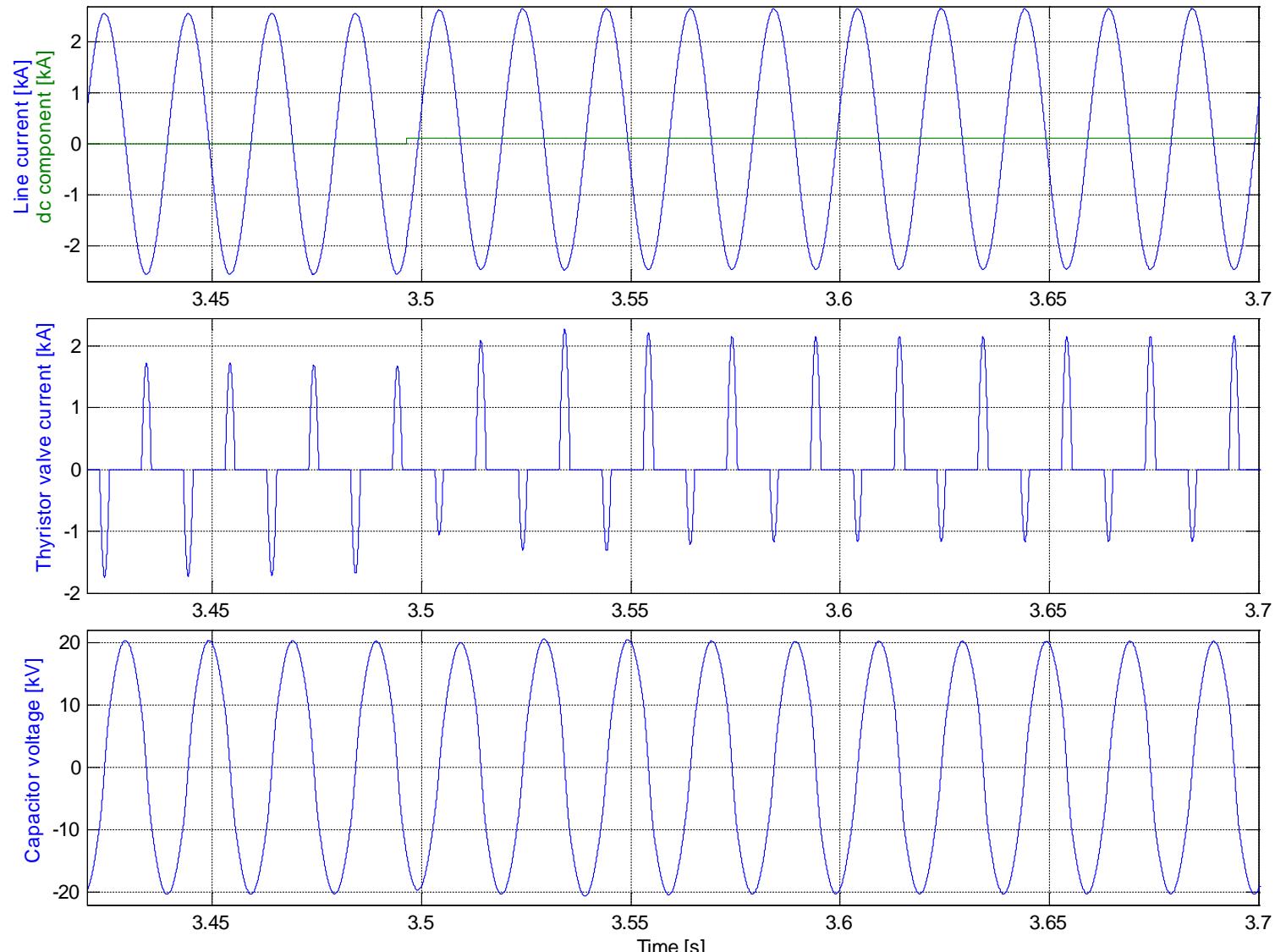


10 Hz current in a TCSC

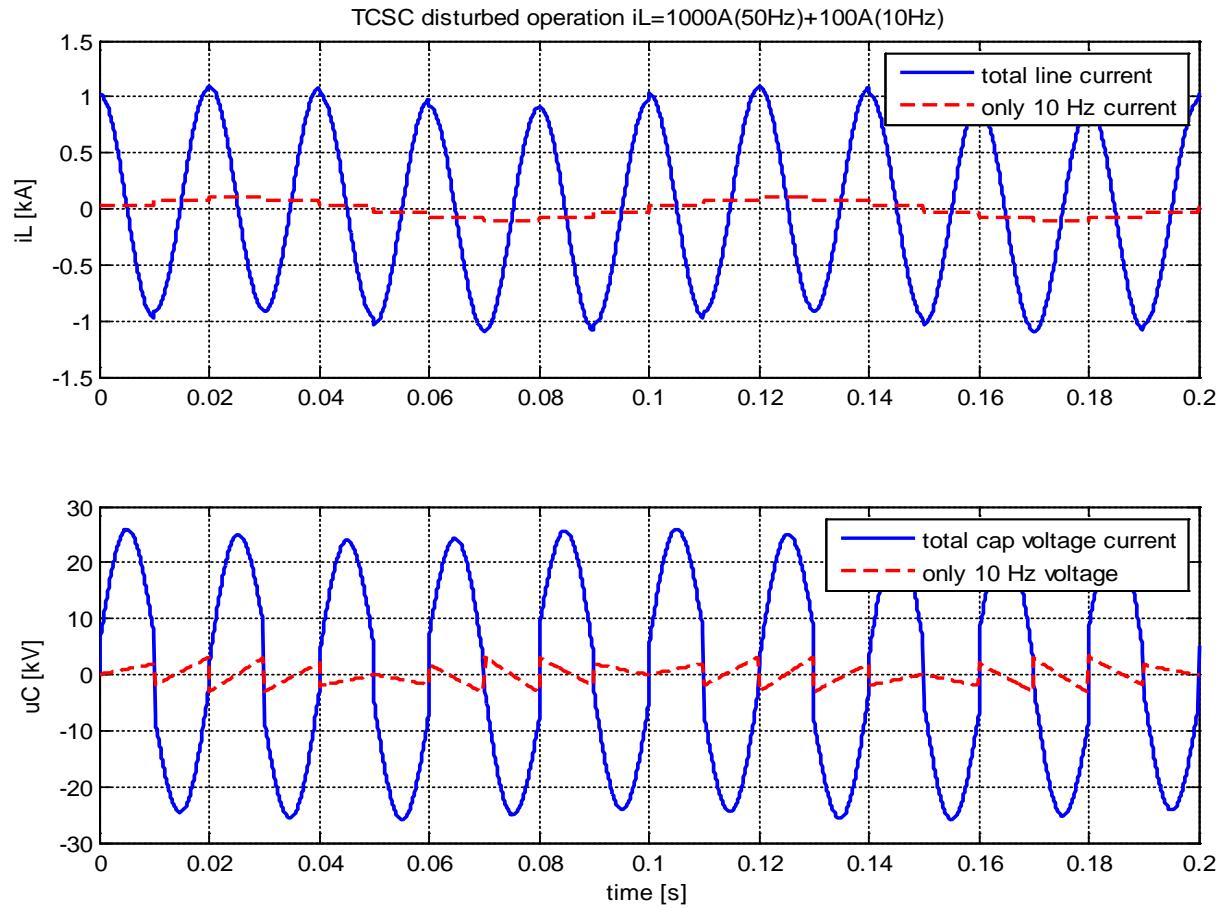


SVR apparent subsynchronous impedance

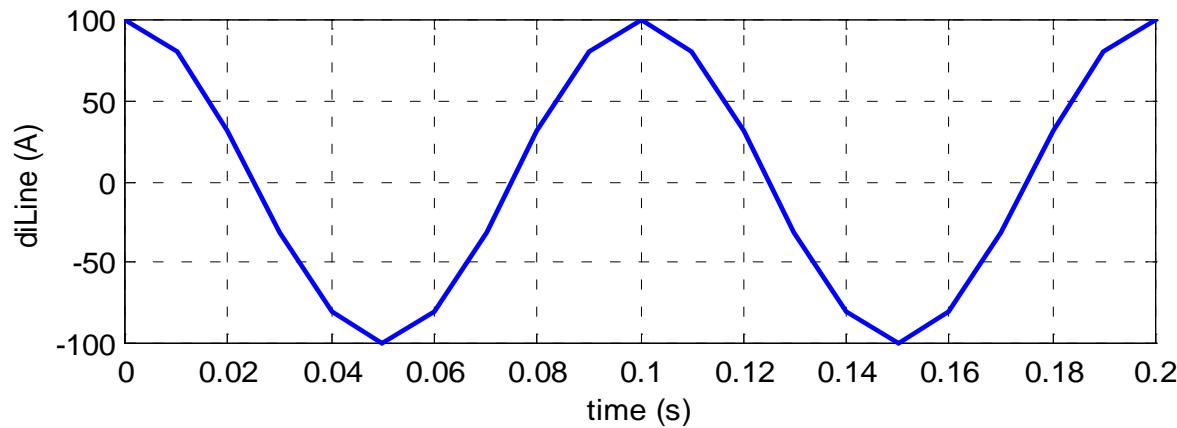


SVR apparent subsynchronous impedance

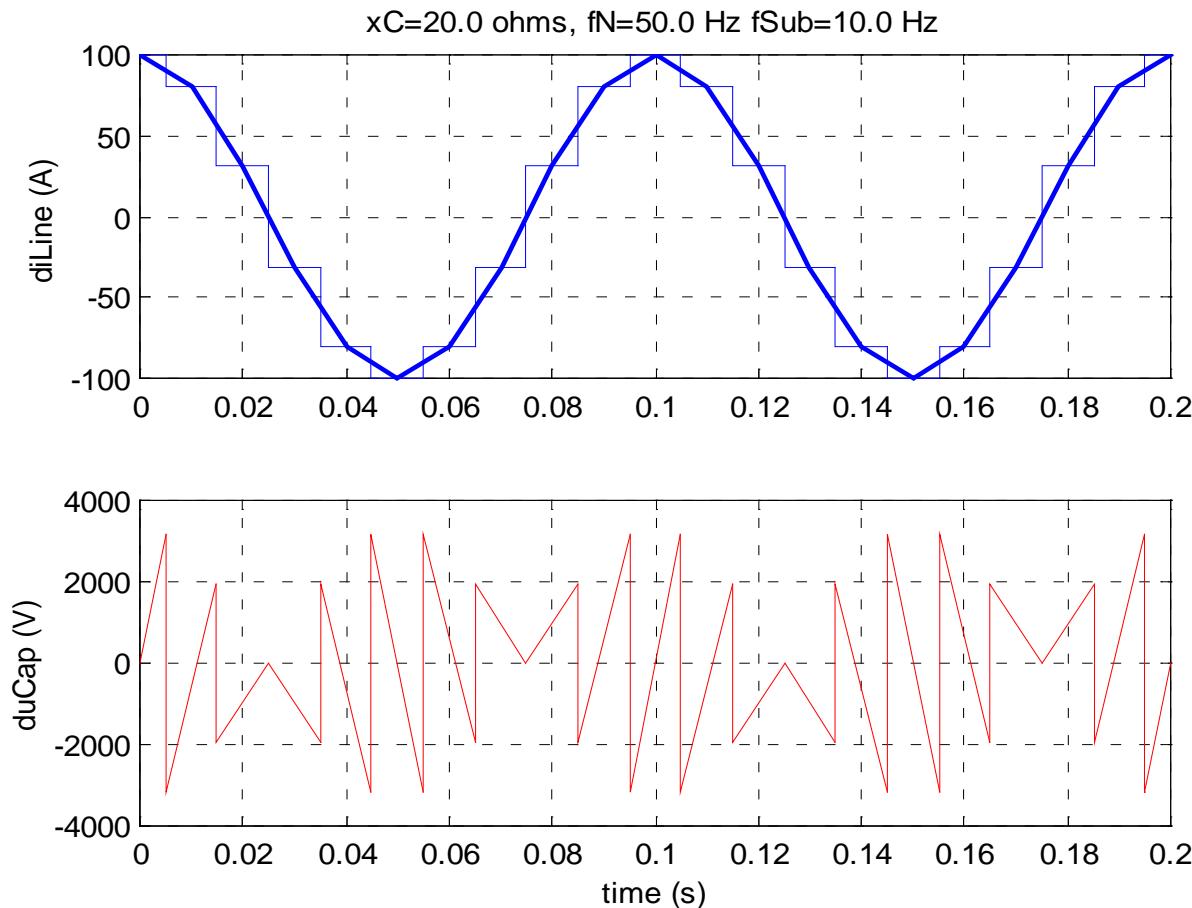

SVR apparent subsynchronous impedance

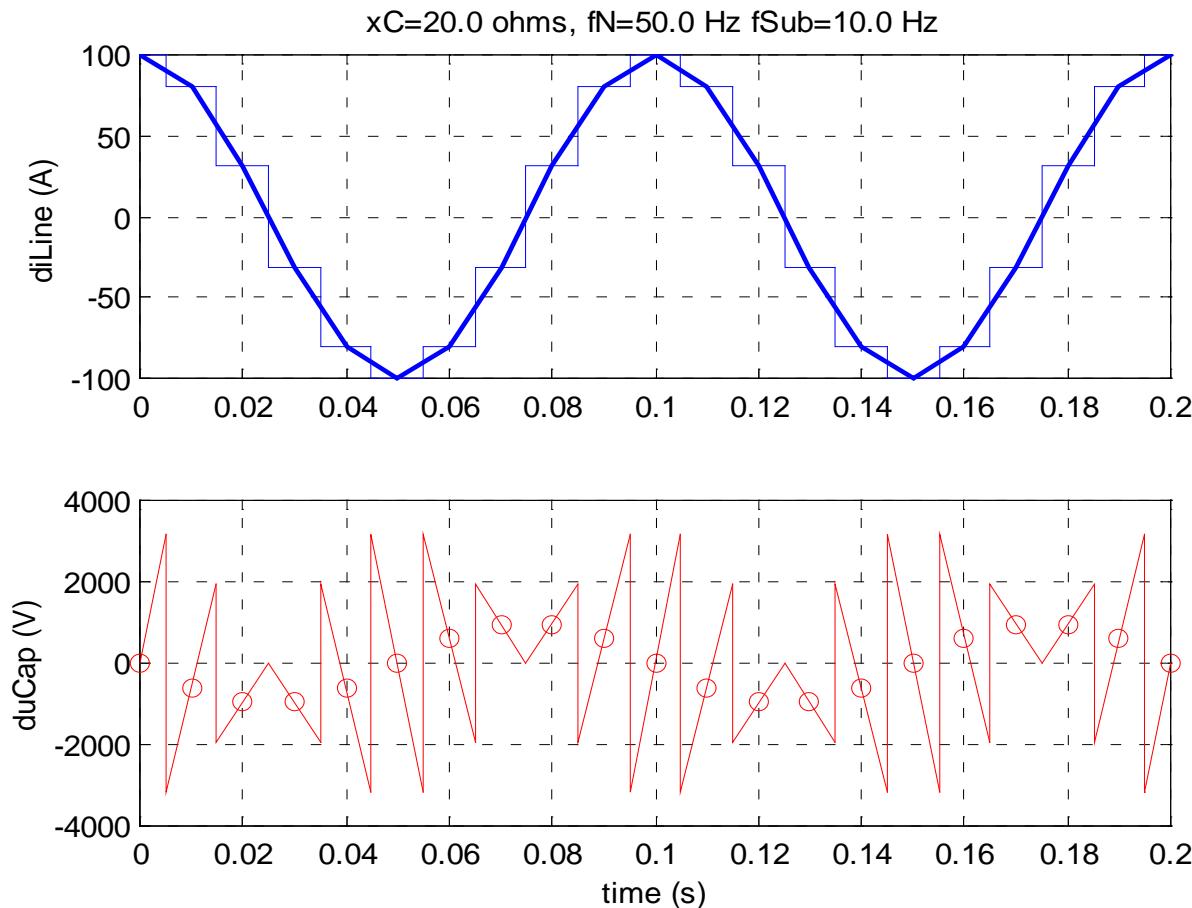


SVR apparent subsynchronous impedance

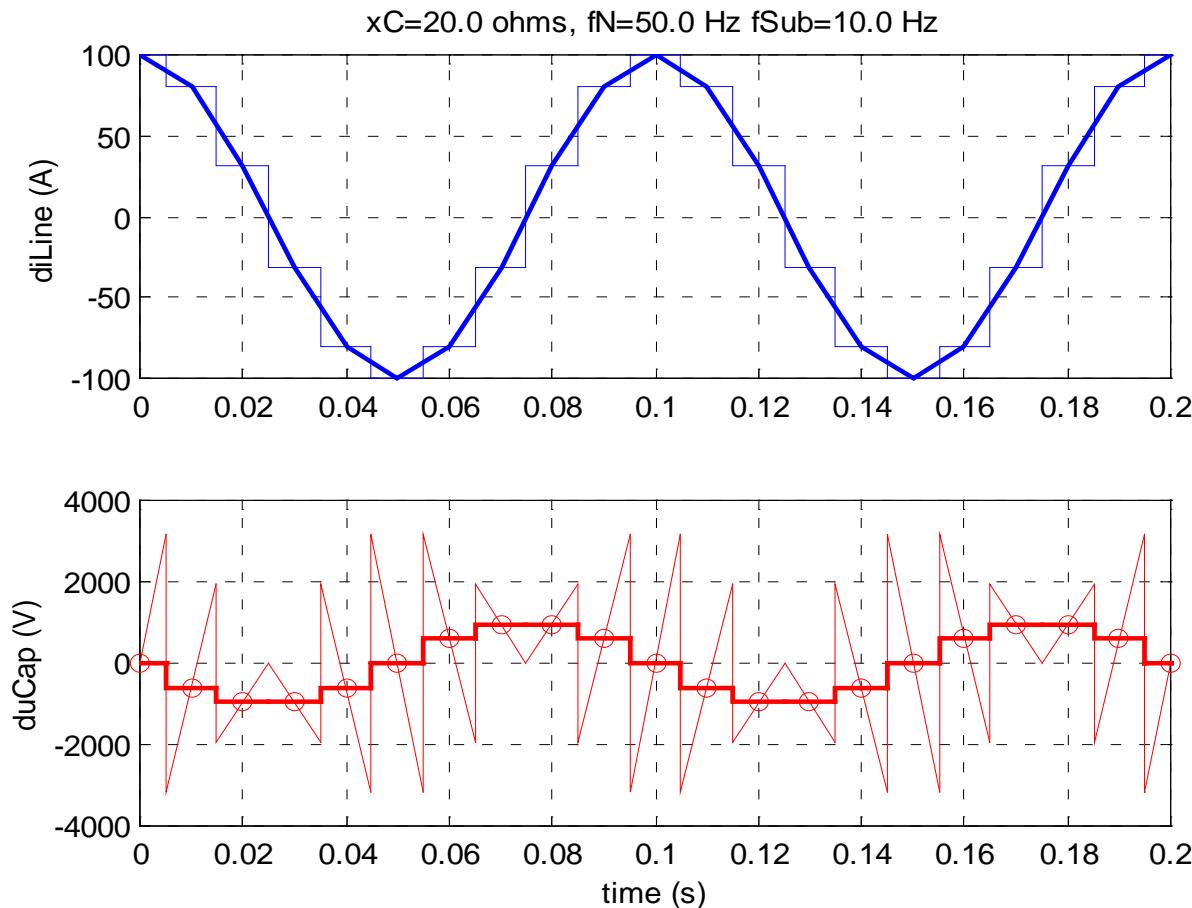


SVR apparent subsynchronous impedance

2 Hz

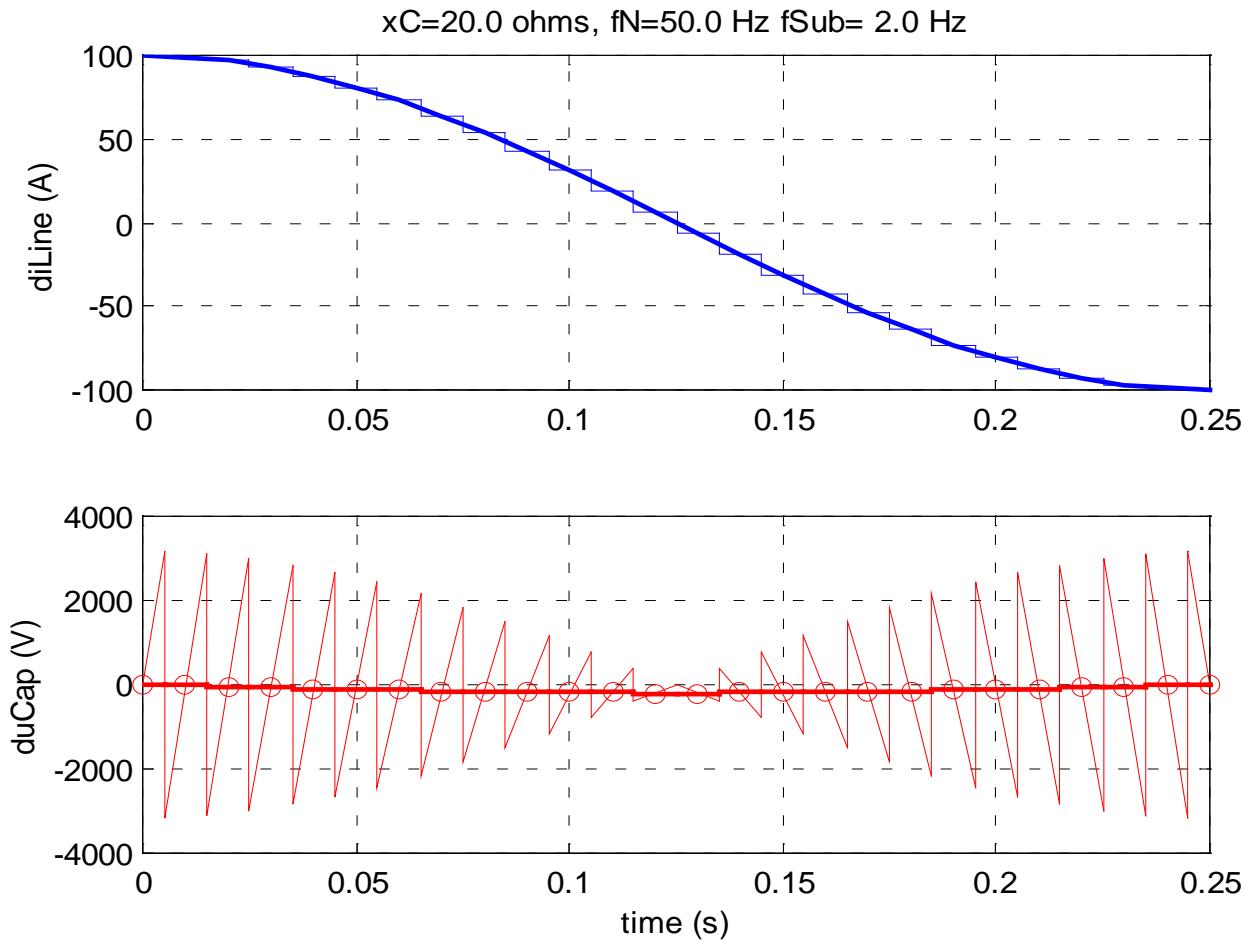


SVR apparent subsynchronous impedance

5 Hz

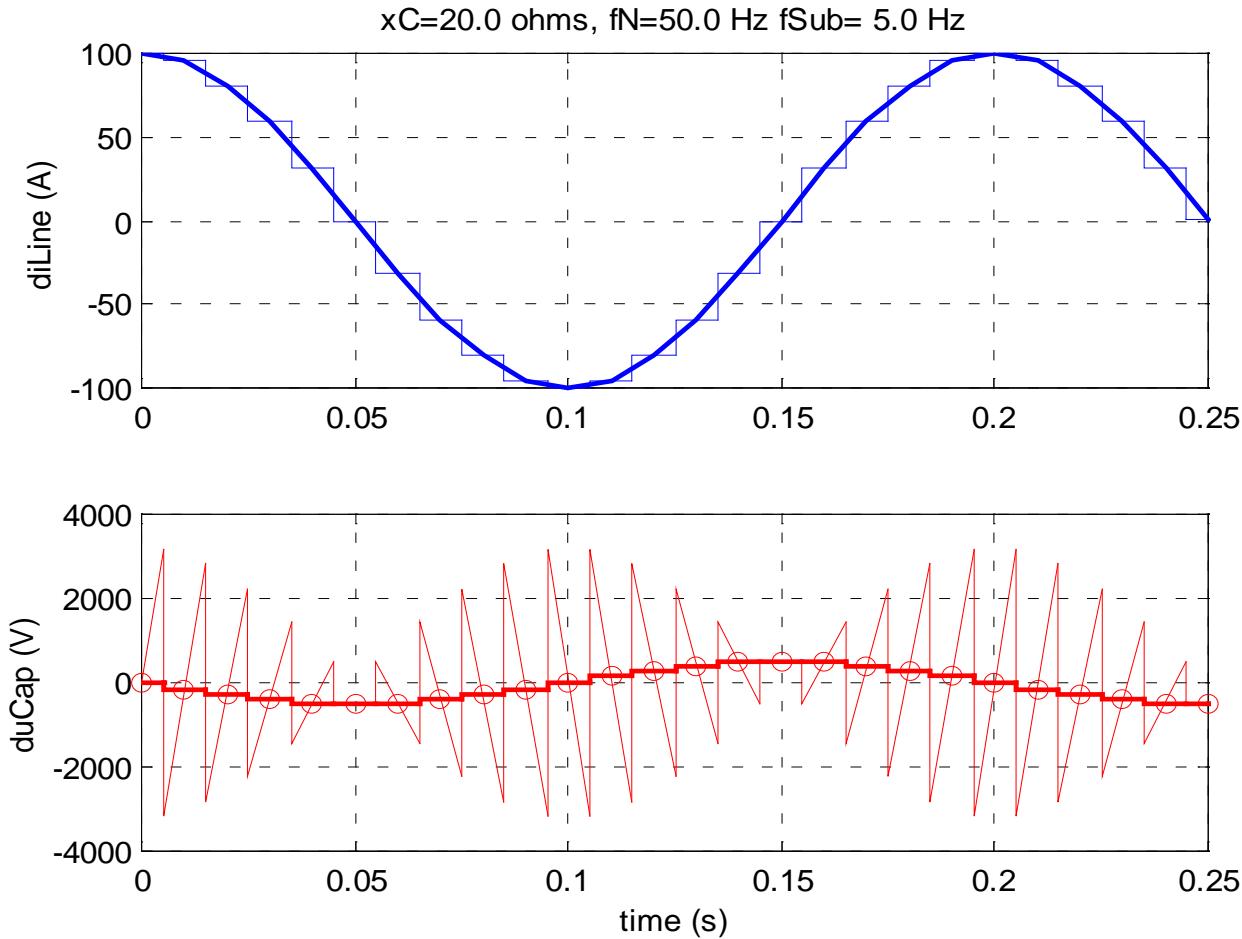


SVR apparent subsynchronous impedance

10 Hz

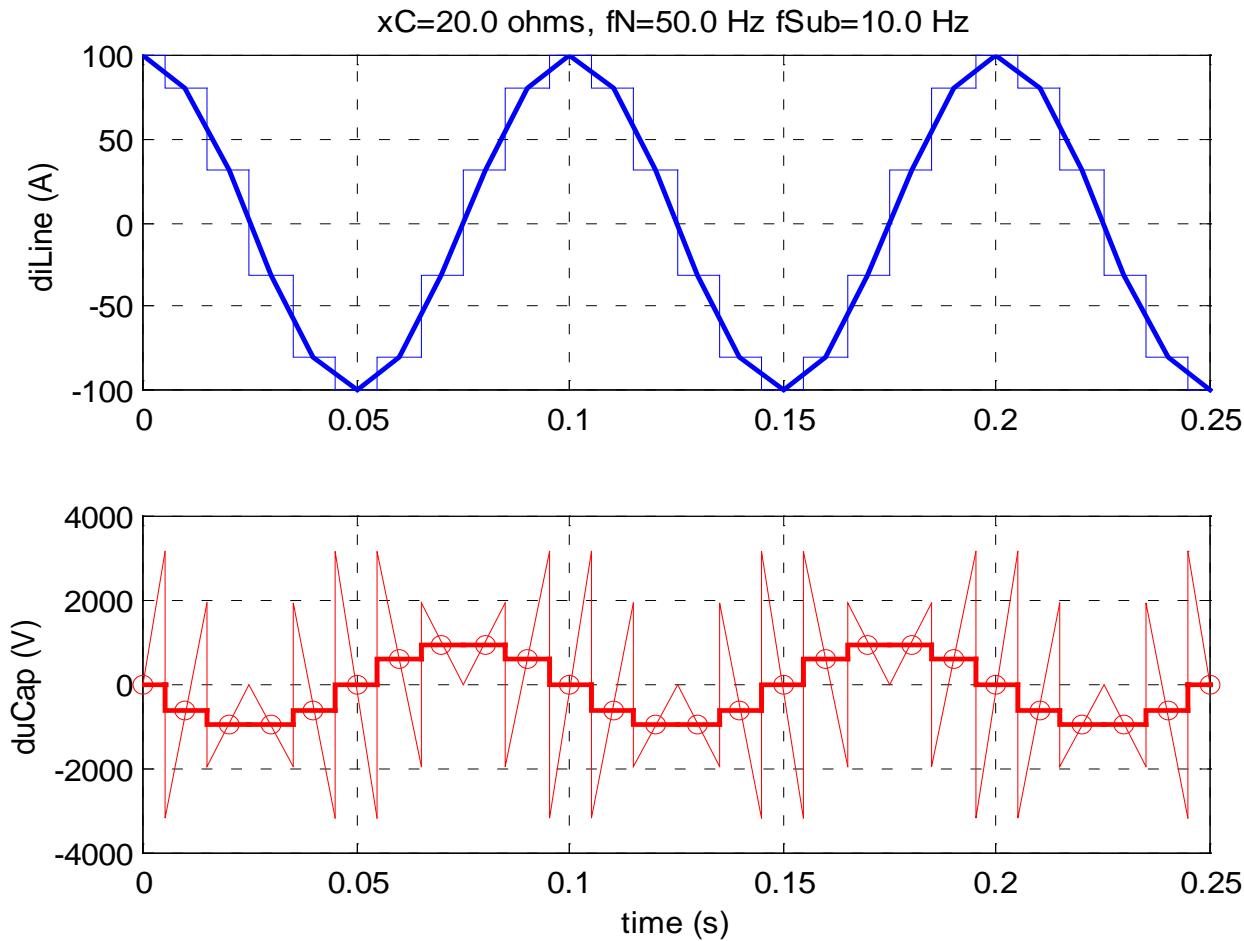


TCSC impedance characteristics

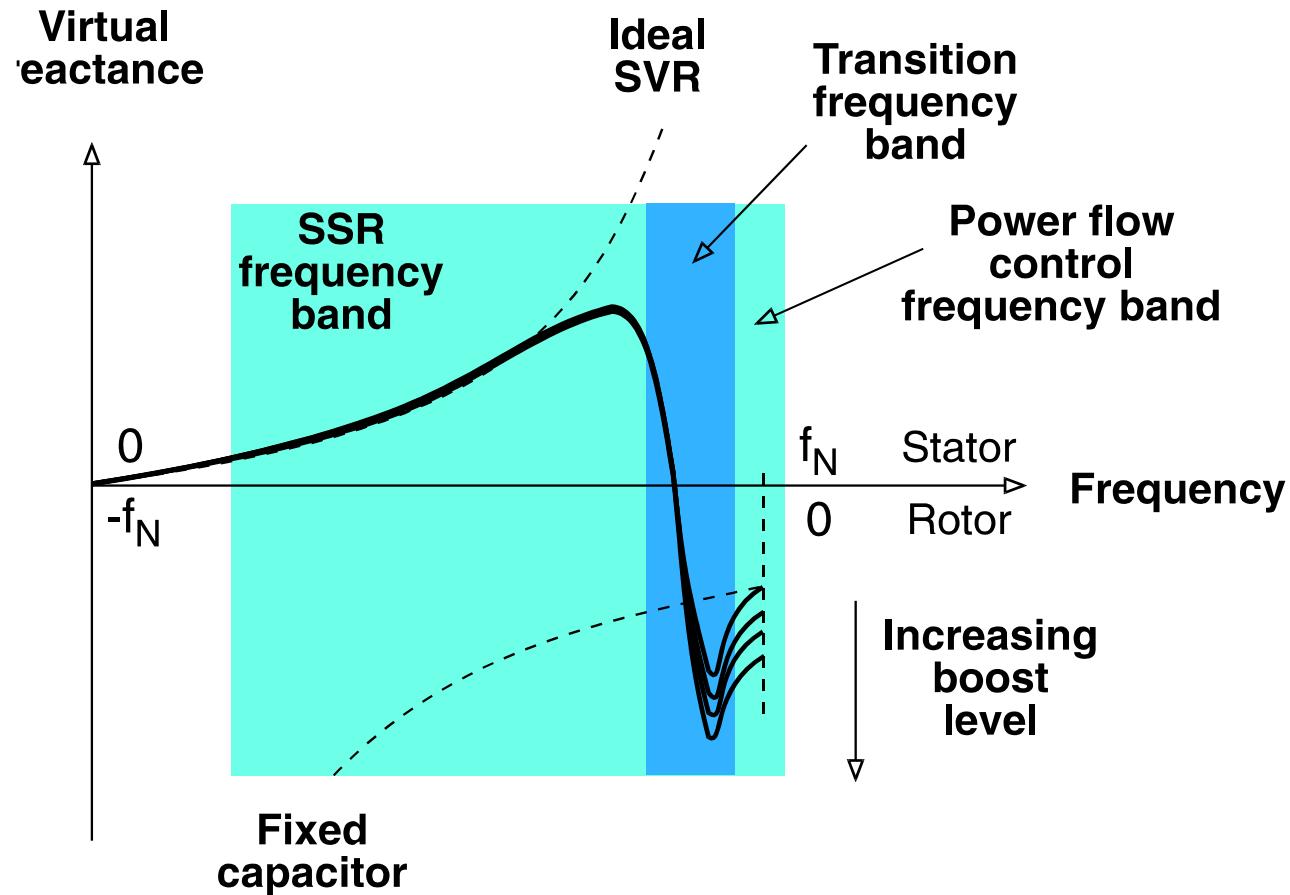

SSR Mitigation Example

TCSC


- Screening Studies

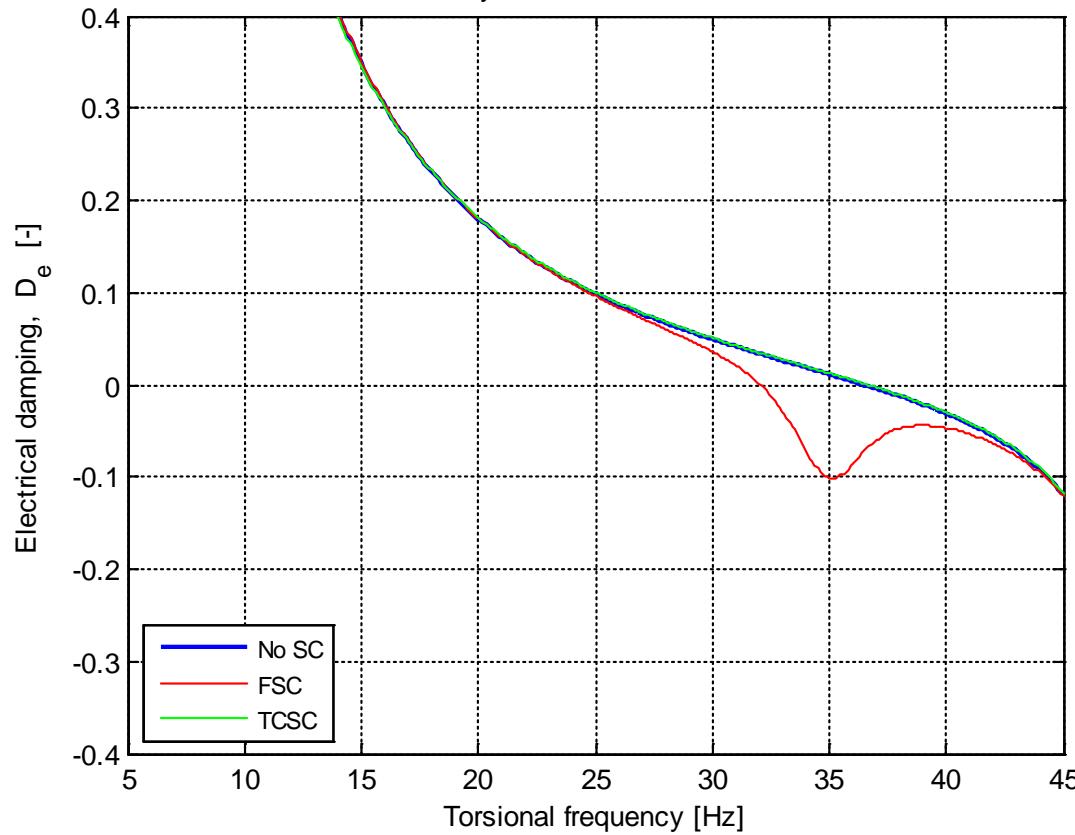

SSR Mitigation Example

TCSC


- RTDS Tests

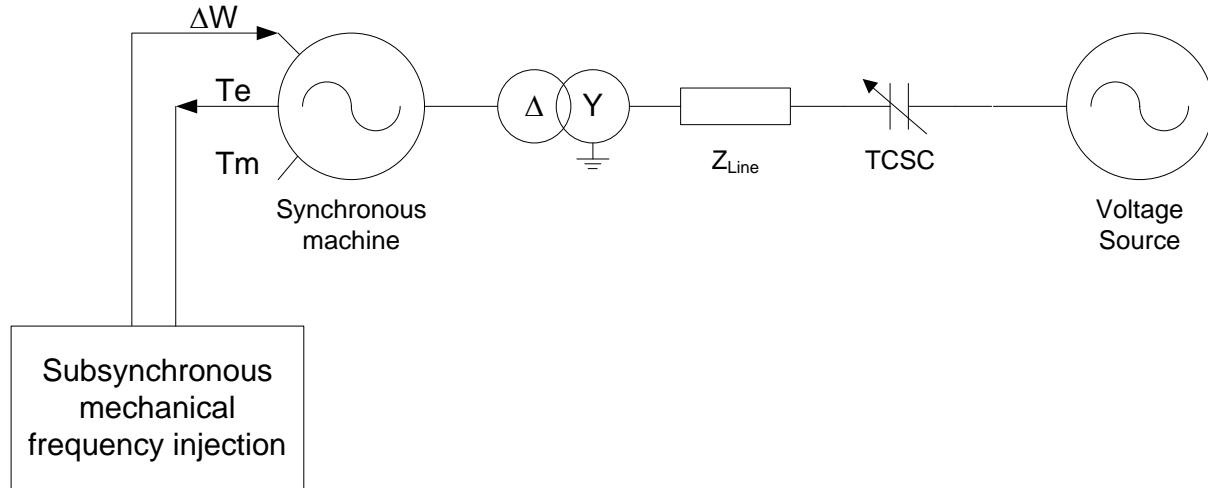

SSR Mitigation Example

TCSC


- RTDS Tests

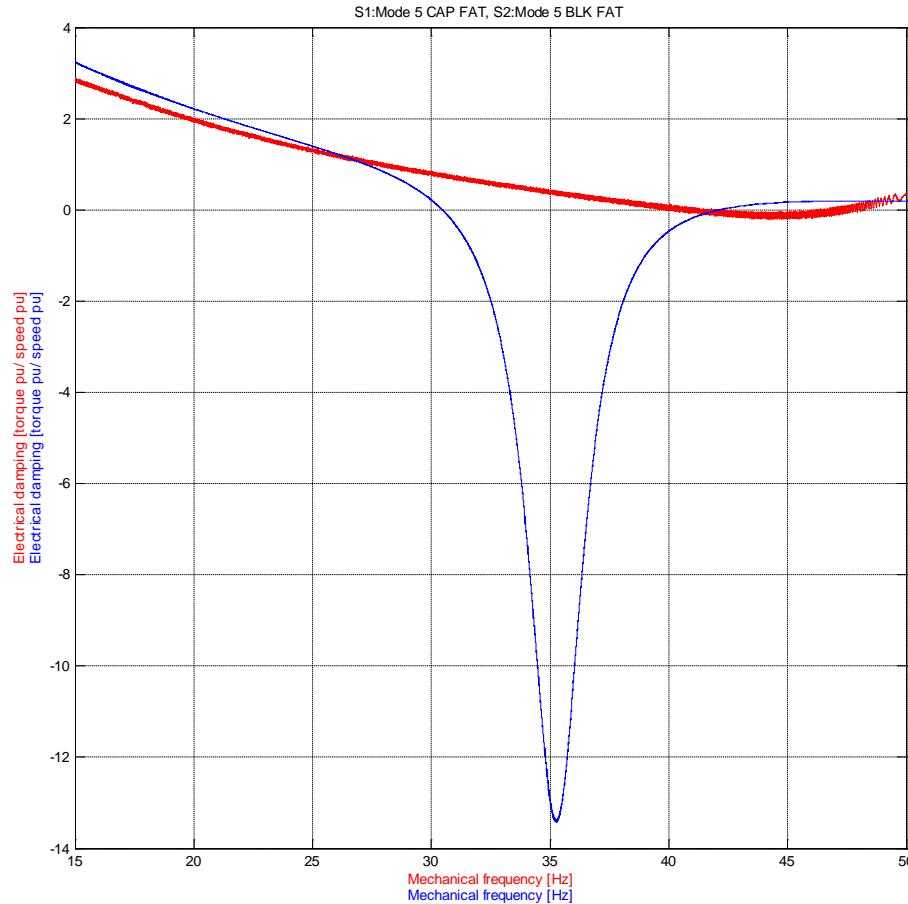

SSR Mitigation Example

TCSC and FSC


- RTDS Tests

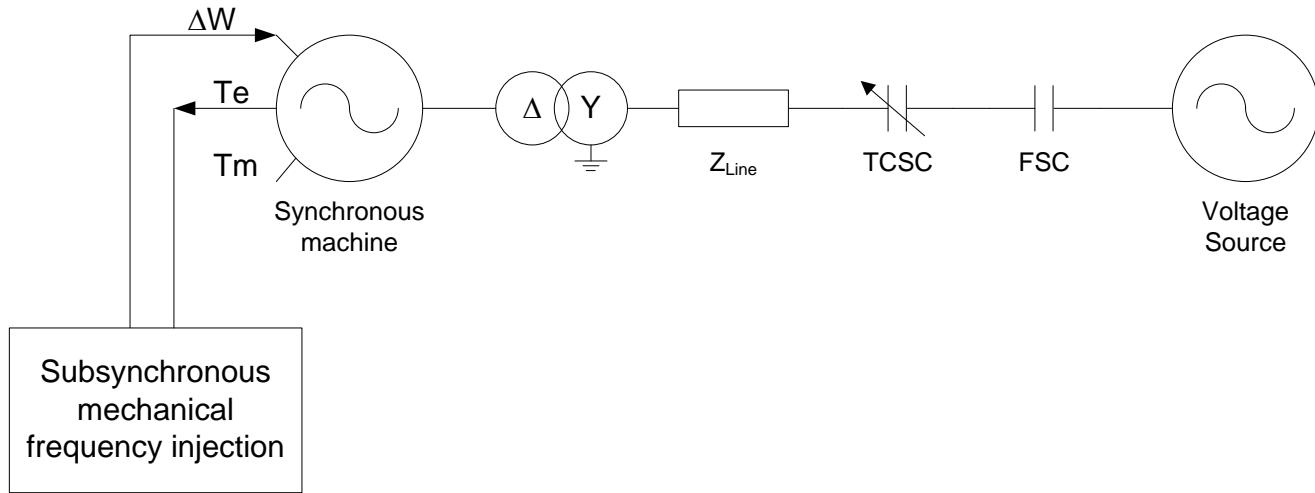

SSR Mitigation Example

TCSC and FSC

- RTDS Tests

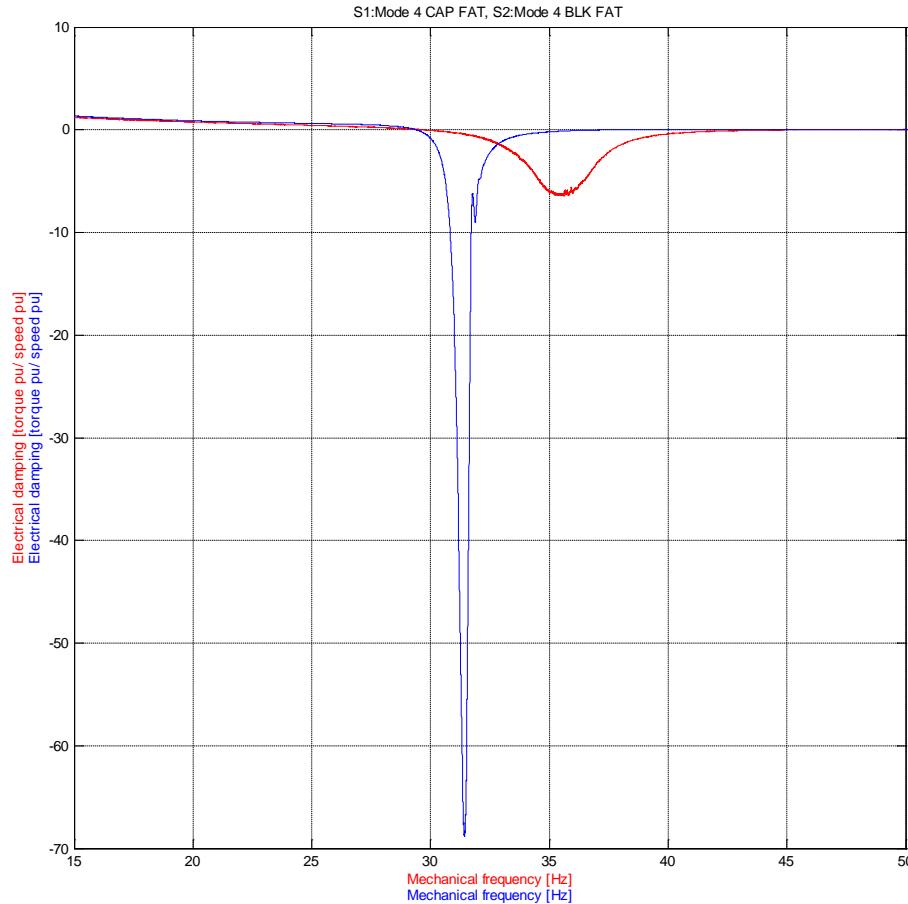

Power and productivity
for a better world™

